



FIGURE 5.33 The complete datapath for the multicycle implementation together with the necessary control lines. The control lines of Figure 5.32 are attached to the control unit, and the control and datapath elements needed to effect changes to the PC are included. The major additions from Figure 5.32 include the multiplexor used to select the source of a new PC value (at the top right); two gates used to combine the PC write signals (top left); and the control signals PCSource, PCWrite, and PCWriteCond. The PCWriteCond signal is ANDed with the Zero output of the ALU to decide whether a branch should be taken; the resulting signal is ORed with the control signal PCWrite to generate the actual write control signal for the PC. In addition, the output of the IR is rearranged to send the lower 26 bits (the jump address) to the logic used to select the next PC. These 26 bits are shifted to the left by two, adding 2 low-order 0 bits; these 28 bits are then concatenated with the high-order 4 bits of the PC, which has already been incremented.

Actions of the 1-bit control signals

Signal name	Effect when deasserted	Effect when asserted
RegDst	The register file destination number for the Write register comes from the rt field.	The register file destination number for the Write register comes from the rd field.
RegWrite	None	The general-purpose register selected by the Write register number is written with the value of the Write data input.
ALUSrcA	The first ALU operand is the PC.	The first ALU operand comes from the A register.
MemRead	None	Content of memory at the location specified by the Address input is put on Memory data output.
MemWrite	None	Memory contents at the location specified by the Address input is replaced by value on Write data input.
MemtoReg	The value fed to the register file Write data input comes from ALUOut.	The value fed to the register file Write data input comes from the MDR.
lorD	The PC is used to supply the address to the memory unit.	ALUOut is used to supply the address to the memory unit.
IRWrite	None	The output of the memory is written into the IR.
PCWrite	None	The PC is written; the source is controlled by PCSource.
PCWriteCond	None	The PC is written if the Zero output from the ALU is also active.

Actions of the 2-bit control signals

Signal name	Value	Effect
ALUOp	00	The ALU performs an add operation.
	01	The ALU performs a subtract operation.
	10	The funct field of the instruction determines the ALU operation.
ALUSrcB	00	The second input to the ALU comes from the B register.
	01	The second input to the ALU is the constant 4.
	10	The second input to the ALU is the sign-extended, lower 16 bits of the IR.
	11	The second input to the ALU is the sign-extended, lower 16 bits of the IR shifted left 2 bits.
PCSource	00	Output of the ALU ($PC + 4$) is sent to the PC for writing.
	01	The contents of ALUOut (the branch target address) are sent to the PC for writing.
	10	The jump target address (IR[25–0] shifted left 2 bits and concatenated with $PC + 4$ [31–28]) is sent to the PC for writing.

FIGURE 5.34 The action caused by the setting of each control signal in Figure 5.33 on page 383. The top table describes the 1-bit control signals, while the bottom table describes the 2-bit signals. Only those control lines that affect multiplexors have an action when they are deasserted. This information is similar to that in Figure 5.18 on page 359 for the single-cycle datapath, but adds several new control lines (IRWrite, PCWrite, PCWriteCond, ALUSrcB, and PCSource) and removes control lines that are no longer used or have been replaced (PCSrc, Branch, and Jump).

ALU operation, or one register file access, or one memory access. With this restriction, the clock cycle could be as short as the longest of these operations.

Recall that at the end of every clock cycle any data values that will be needed on a subsequent cycle must be stored into a register, which can be either one of the major state elements (e.g., the PC, the register file, or the