



**FIGURE 5.17 The datapath of Figure 5.13 with all necessary multiplexers and all control lines identified.** The control lines are shown in color. The ALU control block has also been added. The PC does not require a write control, since it is written once at the end of every clock cycle; the branch control logic determines whether it is written with the incremented PC or the branch target address.